



<b>Year/Semester:</b> I/II	<b>Department :</b> ECE	<b>Unit :</b> I to V
<b>Date:</b> 06.03.2024	<b>Subject Code/Title :</b> EC3251/ Circuit Analysis	<b>Total Hours :</b> 60 Hrs
	<b>Faculty Name :</b> Mrs.A.Karthikeyani	<b>Subject Credit :</b> 4

**Unit-I DC Circuit Analysis**

UNIT-I - DC Circuit Analysis  
Basic Components of electric circuits, Charge, Current, Voltage and Power, Voltage and current Sources, Ohm's law, Kirchoff's current law, Kirchoff's Voltage Law - The single Node - Pair circuits, series and parallel Connected Independent Sources, Resistors in series and parallel, Voltage & current division, Nodal Analysis, Mesh Analysis


Ohm's law:

"The Ratio between potential difference across terminals of a conductor & current through it remains constant, when the physical conditions of the conductor remain unchanged. Here the physical condition is temperature."

$$\frac{V}{I} = \text{constant}$$

$$\frac{V}{I} = R$$

$$V = I \times R$$

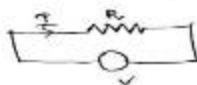

$$P = V \cdot I = I^2 R = \frac{V^2}{R}$$

Charge (Q):

→ The amount of charge passing a point in the circuit

$$Q = I \times t$$


$$[Q = C \cdot V] \quad \text{Capacitor}$$

Problem No: 3

Given that the current is 0.3A. Calculate the charge flowing in the circuit in 20 seconds.

$$Q = 0.3 \times 20 = 6C$$

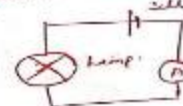P.No: 4: A current of 2A flows thru' a bulb for 3 minutes. Calculate the amount of charge that flows thru' the bulb in this time.




$$Q = 2 \times 180 = 360C \quad [180 = 3 \times 60 \text{ sec}]$$

Current: (I)

$$V = I R \quad [I = V/R]$$

$$I = Q/t$$

$$P = V \times I$$

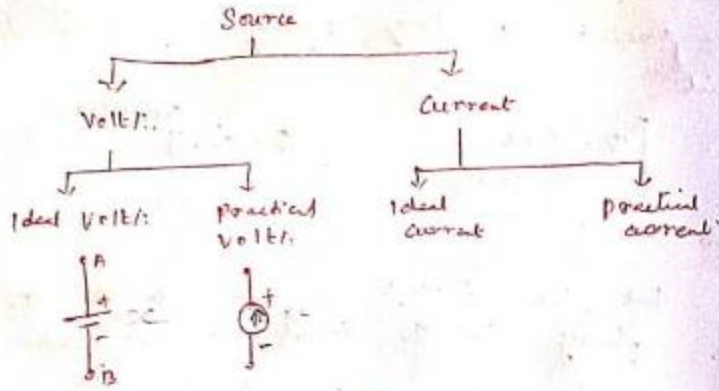


Circuit Responses:

Element	V	I
R (Ω)	$V = IR$	$I = V/R$
L (H)	$V = L \frac{di}{dt}$	$I = \frac{1}{L} \int V dt$
C (F)	$V = \frac{1}{C} \int I dt$	$I = C \frac{dV}{dt}$

Resistors in series & parallel.


Resistor:

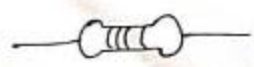⇒ Used to reduce current flow, adjust signal levels, to divide voltages, bias active elements and terminate transmission lines.



⇒ Passive Component  
= Ω (K, M)

Colour Coding:

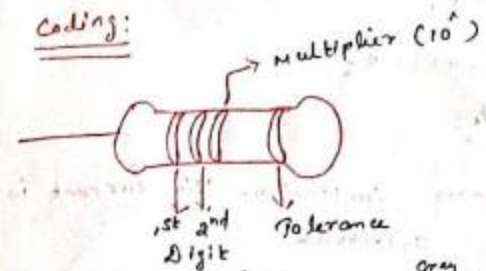

Black	Brown	Red	Orange	Yellow	Green	Blue	Violet	Grey	White
0	1	2	3	4	5	6	7	8	9


±1%, ±2%, ±3%, ±4%, ±5%, ±10%, ±15%, ±20%

Gold: (Multiplier) =  $\times 10^{-1}$ ; Tolerance = ±5%  
Silver: " =  $\times 10^{-2}$ ; " = ±10%

Combinations:

Series [current same, voltage different]  
⇒ If the 'R' connected to end-end, it is said to be series.

Consider the below circuit:

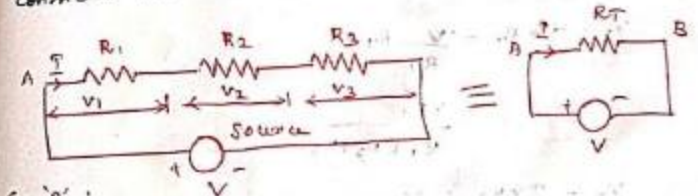

Eq. R:

By ohm's law:

V = Applied voltage

I = source current

$V_1 = IR_1$

$V_2 = IR_2$

$V_3 = IR_3$

∴  $V = V_1 + V_2 + V_3$

$= IR_1 + IR_2 + IR_3 = I(R_1 + R_2 + R_3)$

$$V = I \times R_T$$

$$R_T = R_1 + R_2 + R_3$$

### Salient points:

(1) In the series combination, the current is same

(2) Voltage is distributed

(3)  $R_T >$  Individual 'R'

(4) Powers are additive

$$(5) V = V_1 + V_2 + V_3$$

Voltage drops.

$$(6) R_T = R_1 + R_2 + \dots + R_n$$

### Voltage Division:

$$W.K.T, R_T = R_1 + R_2 + R_3$$

$$I = \frac{V}{R_T} = \frac{V}{R_1 + R_2 + R_3}$$

$$V_1 = I \times R_1 = \frac{V}{R_T} R_1$$

$$= \frac{V R_1}{R_1 + R_2 + R_3}$$

$$V_2 = I \times R_2 = \frac{V}{R_T} R_2 = \frac{V R_2}{R_1 + R_2 + R_3}$$

$$V_3 = I \times R_3 = \frac{V R_3}{R_T} = \frac{V R_3}{R_1 + R_2 + R_3}$$

### Applications:

1. Whenever need of variable volt., var. R<sup>r</sup> (rheostat) is connected in series with the load.

Eg: A fan regulator

2. Decoration lights (min. voltage)

2

### Drawbacks:

⇒ (1) If circuit breaks, no current flow.

(2) Not practicable for lighting circuits. (Lamps = each 25Ω)

(5) The lamps in a set of Christmas tree lights are connected in series. If there are 20 lamps and each lamp has resistance of 25Ω, calculate the total resistance of the set of lamps and hence calculate the current taken from a supply of 230 volts.

### Solution:

$$\text{Supply voltage} = V = 230V$$

$$R = 25\Omega$$

$$n = 20$$


$$R_T = n \times R = 20 \times 25 = 500\Omega$$

$$I = \frac{V}{R_T} = \frac{230}{500} = 0.46A$$

$$\boxed{I = 0.46A}$$
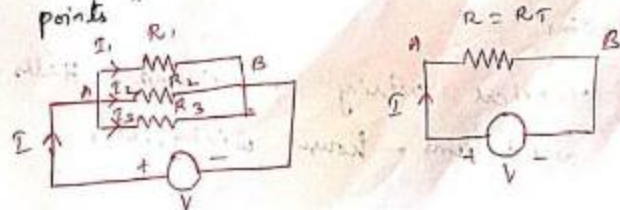
### Parallel:

"If one end of all the resistors is joined to a common point and the other ends are joined to another common point, it is said to be parallel combination between 2 common points"



By ohm's law,

$$I_1 = \frac{V}{R_1} ; I_2 = \frac{V}{R_2} ; I_3 = \frac{V}{R_3}$$

$$I = \frac{V}{R}$$

$$I = I_1 + I_2 + I_3$$

$$\frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\frac{V}{R} = V \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right]$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Salient points:

- (1) 'V' is same across all elements.
- (2) 'I' thru various 'R'  $\neq$  different.
- (3) Total 'R'  $<$  Individual 'R'.
- (4) powers are additive.
- (5) Conductance "

Adv:

- (1) Electrical appliances of diff. power ratings may be rated for the same 'V'.  
Eg: Tube lights, Bulbs, fridge, fan, motor.
- (2) Doesn't affect other branch circuit if a break occur on any of the circuit.

Applications:

- (1) Electrical wiring in cinema Halls, auditoriums, house wiring, etc.,

Current division:

Let, Total current = I

Current thru  $R_1 = I_1$

"  $R_2 = I_2$

$$I_2 R_2 = I_1 R_1$$

$$\therefore I_2 = I_1 \frac{R_1}{R_2}$$

$$\begin{aligned} I &= I_1 + I_2 = I_1 + I_1 \frac{R_1}{R_2} \\ &= I_1 \left( \frac{R_1 + R_2}{R_2} \right) \\ I R_2 &= I_1 (R_1 + R_2) \end{aligned}$$


$$\Rightarrow I_1 = \frac{I R_2}{R_1 + R_2} ; I_2 = \frac{I R_1}{R_1 + R_2}$$

Network Terminology:



Branch:

"A part of the net which connects the various parts of the network with one another"

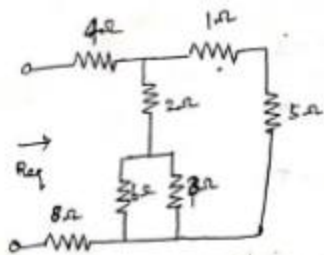
⑥ Find  $R_{eq}$  for the circuit shown in fig.



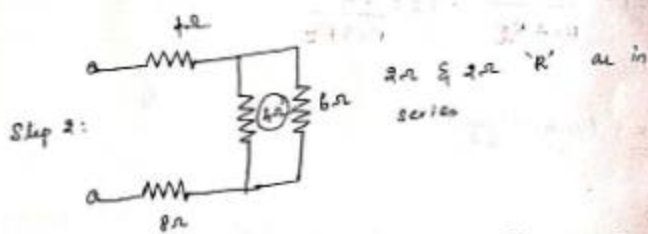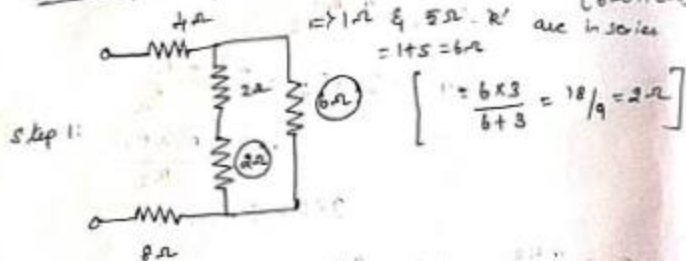Soln:  $\Rightarrow 6\Omega$  &  $3\Omega$  resistors are in parallel.



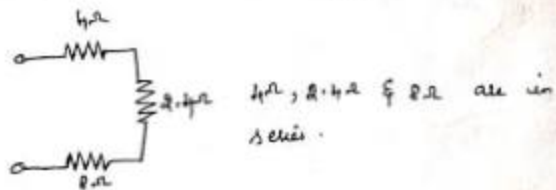
Step 3:  $4\Omega \parallel 6\Omega$  'R'  $\Rightarrow \frac{4 \times 6}{4+6} = \frac{24}{10} = 2.4\Omega$



$\therefore 4 + 2.4 + 8 = 14.4\Omega$

$\therefore R_{eq} = 14.4\Omega$

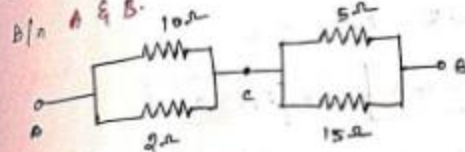⑦ Determine the  $R_{eq}$  of the circuit of fig.




Soln:

Step 1:


$$10\Omega \parallel 2\Omega \quad ; \quad 5\Omega \parallel 15\Omega$$

$$= \frac{10 \times 2}{10+2} \quad ; \quad = \frac{5 \times 15}{5+15}$$
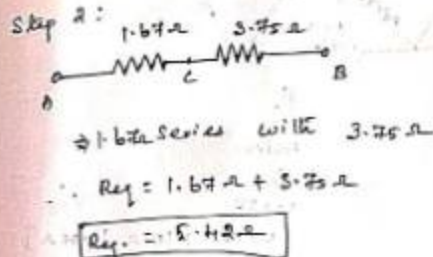
$$= \frac{20}{12} = 1.67\Omega \quad ; \quad = \frac{75}{20} = 3.75\Omega$$




⑧ Find  $R_{eq}$ :

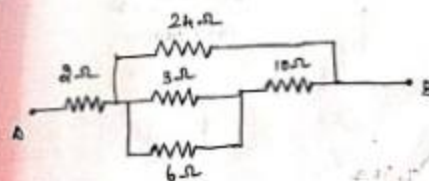


Step 1:
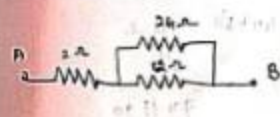
$$3\Omega \parallel 6\Omega = \frac{3 \times 6}{3+6} = \frac{18}{9} = 2\Omega$$



2Ω series with 10Ω

$= 2 + 10 = 12\Omega$

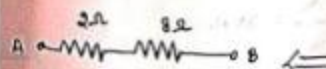

Step 2: Resultant 'R' is in parallel with 24Ω


$\therefore 12 \parallel 24 = \frac{12 \times 24}{12+24} = 8\Omega$

Step 3:

2  $\Omega$  series with  $8 \Omega = 10 \Omega$

$$\therefore R_{eq} = 10 \Omega \quad (\text{or}) \quad R_{AB} = 10 \Omega$$

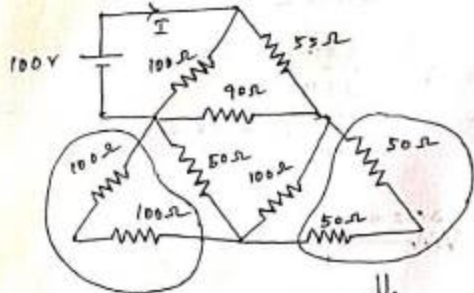Ⓔ Find the total current taken from the source.



Step 1:


Series  
↓  
 $100 + 100$   
[  $200 \parallel 100$  ] =  $200 \Omega$

↓  
 $= \frac{200 \times 50}{200 + 50} = 40$

Series.  
↓  
 $50 + 50$   
 $= 100 \Omega$  [  $100 \Omega \parallel 100 \Omega$  ]

↓  
 $= \frac{100 \times 100}{100 + 100} = 50$

Step 2:

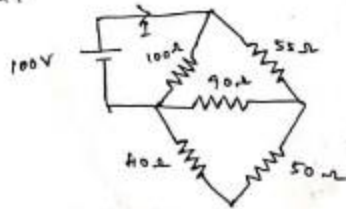

40  $\Omega$  series with 50  $\Omega = 40 + 50 = 90 \Omega$

90  $\parallel$  90

$$\therefore \frac{90 \times 90}{90 + 90} = \frac{8100}{180} = 45 \Omega$$

Step 3:




$$\frac{45 \times 55}{45 + 55} = \frac{2475}{100} = 24.75$$

45  $\Omega$  series with 55  $\Omega = 45 + 55 = 100 \Omega$

$$100 \Omega \parallel 100 \Omega = \frac{100 \times 100}{100 + 100} = 50 \Omega$$

$$\therefore R_{eq} = 50 \Omega$$


Step 2:

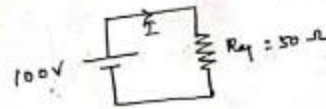


$$I = \frac{V}{R_{eq}} = \frac{100}{50} = 2 \text{ A}$$

$$\therefore \text{Total current} = 2 \text{ A}$$


Practise Problem: Find  $R_T$

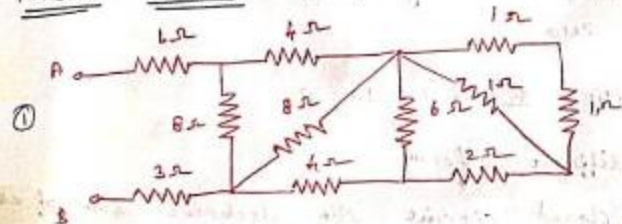

②

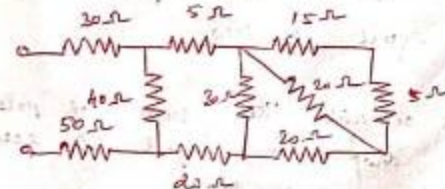

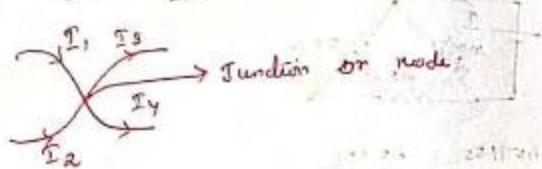Kirchoff's current law (KCL) [K's first law]



"The algebraic sum of current meeting at a junction (or) node is equal to zero."

Let  $I_1, I_2, I_3$  &  $I_4 \Rightarrow$  current flow through the conductors.

∴ current entering +ve  
current leaving -ve

$$I_1 + I_2 - I_3 - I_4 = 0$$

$$\therefore I_1 + I_2 = I_3 + I_4$$

$$\boxed{\text{Current entering} = \text{current leaving}}$$

Kirchoff's Voltage Law (KVL) [K's second law]

"The algebraic sum of electromotive forces plus the algebraic sum of voltage across the impedances, in any closed electrical circuit is equal to zero."

$$\text{Mathematically, } \sum \text{emf} + \sum I R = 0$$

Statement in different forms:

In any closed circuit, the algebraic sum of the voltage is equal to zero.


(or)

In a closed circuit, the sum of potential rise & potential drop is equal to zero.

(or)

In any closed circuit (or) closed loop, the sum of potential rise is equal to potential drop.

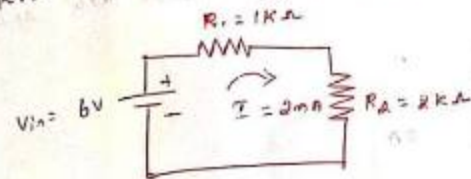10. For the given circuit in figure, check whether KVL is verifying or not.



Voltage across  $R_1$ ;  $V_1 = I R_1 = 2 \times 10^{-3} \times 1 \times 10^3$   
 $= 2 \text{ V}$

Voltage across  $R_2$ ;  $V_2 = I R_2 = 2 \times 10^{-3} \times 2 \times 10^3$   
 $= 4 \text{ V}$

∴ potential rise  $V_{in} = V_1 + V_2$   
 $= 2 + 4$   
 $= 6 \text{ V}$

Hence KVL is verified.

11. In the circuit shown in figure, calculate

- (i) The current in other resistors.
- (ii) The value of unknown resistance 'x'.
- (iii) Req. across A-B.



Solution: (Hint: All the R are in parallel  $\rightarrow$  V)

(i) Given a current thru'  $6\Omega = 5A$

$\therefore$  'V' across  $6\Omega = 5 \times 6 = 30V$  [Ohm's law]  
 Again, by Ohm's law, the current thru'

$$I_{30} = \frac{30}{30} = 1A$$

$$I_{15} = \frac{30}{15} = 2A$$

$$I_6 = 5A$$

By KCL:

$$I = I_6 + I_x + I_{30} + I_{15}$$

$$10 = 5 + I_x + 1 + 2$$

$$I_x = 2A$$

(ii)  $\therefore x = \frac{30}{2} = 15\Omega$

(iii)  $R_{eq}$ :

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$

$$= \frac{1}{6} + \frac{1}{15} + \frac{1}{30} + \frac{1}{15}$$

$$\frac{1}{R_{eq}} = \frac{1}{3} \Rightarrow R_{eq} = 3\Omega$$

$\therefore$  Ans: (i)  $I_x = 2A$ ;  $I_{30} = 1A$ ;  $I_{15} = 2A$


(ii)  $x = 15\Omega$

(iii)  $R_{eq} = R_{eq} = 3\Omega$

(1A) 3 resistors of  $6\Omega$ ,  $9\Omega$  &  $15\Omega$  are connected in parallel to a  $18V$  supply. Calculate

- (a) the current in each branch of the network
- (b) the supply current
- (c) the total resistance of the network.

Solution:

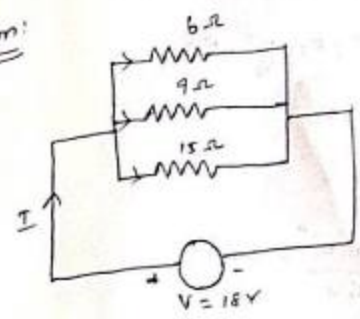

(a)  $\therefore$  current in each branch:

By Ohm's law applied to each 'R',

$$I_6 = \frac{18}{6} = 3A$$

$$I_9 = \frac{18}{9} = 2A$$

$$I_{15} = \frac{18}{15} = \frac{6}{5} = 1.2A$$

(b)  $\therefore$  By KCL,

Supply current = Source current

$$I_{source} = I_6 + I_9 + I_{15}$$

$$= 3 + 2 + 1.2$$

$$= 6.2A$$

(c)

$$R_{eq} = \frac{V}{I_{source}} = \frac{18}{6.2} = 2.9\Omega$$

$$R = 2.9\Omega$$

$$\left( \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$= \frac{1}{6} + \frac{1}{9} + \frac{1}{15}$$

$$= 2.903$$



Practical problems:

① A parallel network consists of 3 resistors  $4\Omega$ ,  $8\Omega$  &  $32\Omega$ . If the current in the resistor is  $2A$ , what are the currents in other resistors? Ans:  $I_1 = 4A$ ;  $I_2 = 0.5A$ .

Since the resistors are connected in parallel, voltage across them is the same.

Soln: i.e.,  $I_1 R_1 = I_2 R_2 = I_3 R_3$


$$I_1 R_1 = I_2 R_2$$

$$I_1 = \frac{I_2 R_2}{R_1}$$


$$I_1 = \frac{2 \times 8}{4} = 4A$$

$$I_3 R_3 = I_2 R_2$$

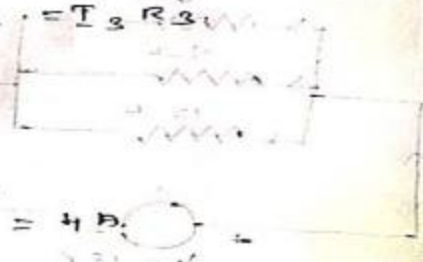
$$I_3 = \frac{I_2 R_2}{R_3} = \frac{2 \times 8}{32} = 0.5A$$



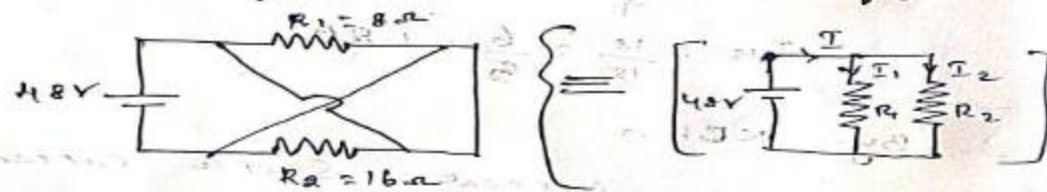
② Calculate the current supplied by the battery in the given circuit of the fig.



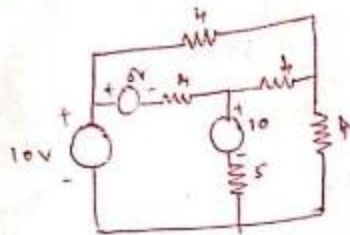14. Find the current flowing through  $5\Omega$  resistor for the circuit below by using mesh analysis.



Soln:

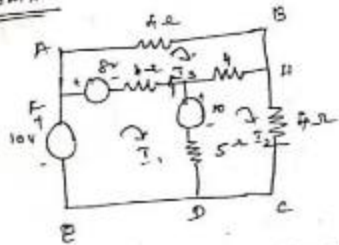

Apply KVL to loop 1 (F G D E F),

$$-10 + 8 + 4(I_1 - I_3) + 10 + 5(I_1 - I_2) = 0$$

$$9I_1 - 5I_2 - 4I_3 = 0 \quad \text{--- (1)}$$

Apply KVL to loop 2 (G H C D G)

$$4(I_2 - I_3) + 4I_2 + 5(I_2 - I_1) - 10 = 0$$

$$-5I_1 + 13I_2 - 4I_3 = 10 \quad \text{--- (2)}$$

Apply KVL to loop 3 (A B H G F A)

$$4I_3 + 4(I_3 - I_2) + 4(I_3 - I_1) - 8 = 0$$

$$-4I_1 - 4I_2 + 12I_3 = 8 \quad \text{--- (3)}$$

$$\Rightarrow I_1 + I_2 - 3I_3 = -2 \quad \text{--- (4)}$$

Cramer's Rule,  
 $I_1 = \frac{D_1}{D}; I_2 = \frac{D_2}{D}$  [We need to find  $\Delta$  &  $I$  across  $5\Omega$  resistor]

$$\begin{bmatrix} 9 & -5 & -4 \\ -5 & 13 & -4 \\ -4 & -4 & 12 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} -8 \\ 10 \\ 8 \end{bmatrix}$$

So,  $I_1, I_2, I_3$  is enough

$$\therefore I_1 = \frac{D_1}{\Delta} = \frac{592}{592} = 0.364 \text{ A}$$

$$I_2 = \frac{760}{592} = 1.283 \text{ A}$$


$$\therefore I_2 - I_1 = 1.283 - 0.364 = 0.919 \text{ A}$$

The total  $I_3 = 0.919 \text{ A}$


Nodal Analysis:

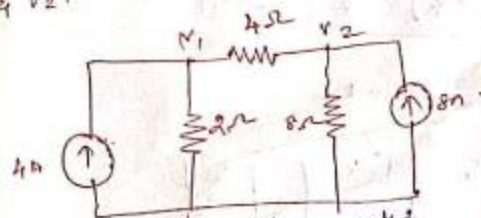15. Find the node voltages in the given circuit using nodal method (or) nodal analysis.

Cons  
 Write the node equilibrium equation after the networks shown below. Also find the node voltages  $V_1$  &  $V_2$ .



Solution:

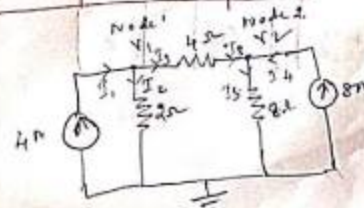

Apply KCL at node ①,

Current entering  $\sum$  leaving  $\sum$  at node 1,

$$I_1 - I_2 - I_3 = 0$$

$$4 - \left(\frac{V_1 - 0}{2}\right) - \left(\frac{V_1 - V_2}{4}\right) = 0$$

$$4 - \frac{V_1}{2} - \frac{V_1}{4} + \frac{V_2}{4} = 0$$

$$-\left(\frac{1}{2} + \frac{1}{4}\right)V_1 + \frac{V_2}{4} = -4$$

$$\boxed{\left(\frac{3}{4} + \frac{1}{4}\right)V_1 - \frac{V_2}{4} = 4} \rightarrow \text{①}$$

Apply KCL at node ②,

$$I_3 - I_5 + I_4 = 0$$

$$\frac{V_1 - V_2}{4} - \left(\frac{V_2 - 0}{8}\right) + 8 = 0$$

$$\frac{V_1}{4} - \frac{V_2}{4} - \frac{V_2}{8} + 8 = 0$$

$$\left(\frac{1}{4}\right)V_1 - \left(\frac{1}{4} + \frac{1}{8}\right)V_2 = -8$$

(or)

$$\boxed{-\left(\frac{1}{4}\right)V_1 + \left(\frac{1}{4} + \frac{1}{8}\right)V_2 = 8} \rightarrow \text{②}$$

In matrix format,

$$\begin{bmatrix} \frac{3}{2} + \frac{1}{4} & -\frac{1}{4} \\ -\frac{1}{4} & \frac{1}{4} + \frac{1}{8} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 4 \\ 8 \end{bmatrix}$$

By Grammer's Rule,

$$V_1 = \frac{\Delta_1}{\Delta}; V_2 = \frac{\Delta_2}{\Delta}$$

$$\Delta = \begin{vmatrix} \frac{3}{2} + \frac{1}{4} & -\frac{1}{4} \\ -\frac{1}{4} & \frac{1}{4} + \frac{1}{8} \end{vmatrix} = \begin{vmatrix} \frac{3}{4} & -\frac{1}{4} \\ -\frac{1}{4} & \frac{3}{8} \end{vmatrix}$$

$$= \frac{3}{4} \left(\frac{3}{8}\right) - \left(-\frac{1}{4}\right)\left(-\frac{1}{4}\right) = \frac{9}{32} - \frac{1}{16} = \frac{9-2}{32} = \frac{7}{32}$$

$$= 0.22$$

$$\Delta_1 = \begin{vmatrix} 4 & -\frac{1}{4} \\ 8 & \frac{3}{8} \end{vmatrix} = 4\left(\frac{3}{8}\right) - \left(-\frac{1}{4}\right)(8) = \frac{12}{8} + \frac{8}{4} = \frac{12+16}{8} = \frac{28}{8} = 3.5$$

$$\Delta_2 = \begin{vmatrix} \frac{3}{4} & 4 \\ -\frac{1}{4} & 8 \end{vmatrix} = \frac{3}{4}(8) - 4\left(-\frac{1}{4}\right) = \frac{24}{4} + \frac{4}{4} = 7$$


$$\therefore V_1 = \frac{\Delta_1}{\Delta} = \frac{3.5}{0.22} = 15.9 \text{ V}$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{7}{0.22} = 31.82 \text{ V}$$


Node voltages:

$$\therefore V_1 = 15.9 \text{ V}; V_2 = 31.82 \text{ V}$$

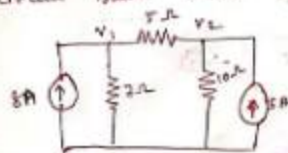- 1b. Find the current flowing through each 'R' for the circuit shown below by nodal analysis.



Soln:

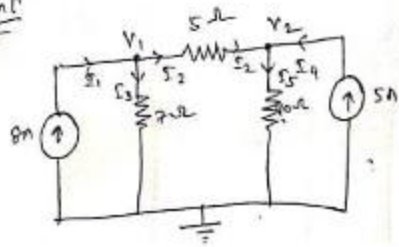

Apply KCL at node 1,

$$I_1 - I_2 - I_3 = 0$$

$$8 - \left(\frac{V_1 - V_2}{5}\right) - \frac{V_1}{7} = 0$$

$$8 - \frac{V_1}{5} + \frac{V_2}{5} - \frac{V_1}{7} = 0$$

$$\left(\frac{1}{5} + \frac{1}{7}\right)V_1 + \frac{V_2}{5} = 8$$

$$\left(\frac{1}{5} + \frac{1}{7}\right)V_1 - \frac{V_2}{5} = 8 \rightarrow \textcircled{1}$$

Apply KCL at node 2,

$$I_2 + I_4 - I_5 = 0$$

$$\frac{V_1 - V_2}{5} + 5 - \frac{V_2}{10} = 0$$

$$\frac{V_1}{5} - \frac{V_2}{5} + 5 - \frac{V_2}{10} = 0$$

$$\frac{V_1}{5} - \left(\frac{1}{5} + \frac{1}{10}\right)V_2 = -5$$

$$-\frac{V_1}{5} + \left(\frac{1}{5} + \frac{1}{10}\right)V_2 = 5 \rightarrow \textcircled{2}$$

Matrix formation,

$$\begin{bmatrix} \frac{1}{5} + \frac{1}{7} & -\frac{1}{5} \\ -\frac{1}{5} & \frac{1}{5} + \frac{1}{10} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 8 \\ 5 \end{bmatrix}$$

$$D = \begin{vmatrix} \frac{1}{5} + \frac{1}{7} & -\frac{1}{5} \\ -\frac{1}{5} & \frac{1}{5} + \frac{1}{10} \end{vmatrix} = \begin{vmatrix} \frac{12}{35} & -\frac{1}{5} \\ -\frac{1}{5} & \frac{3}{10} \end{vmatrix}$$

$$= \frac{12}{35} \left(\frac{3}{10}\right) - \left(-\frac{1}{5}\right)\left(-\frac{1}{5}\right) = \frac{36}{350} - \frac{1}{25}$$

$$D = 0.0628$$

$$\therefore D_1 = 3.4; D_2 = 8.314$$

$$V_1 = \frac{3.4}{0.0628} = 54.14 \text{ V}$$

$$V_2 = \frac{8.314}{0.0628} = 52.22 \text{ V}$$

At: at each R's,  
current thru' 5A,


$$I_2 = \frac{V_1 - V_2}{5} = \frac{54.14 - 52.22}{5} = 0.274 \text{ A}$$

$$I_2 = 0.274 \text{ A}$$

$$I_3 = \frac{V_1}{7} = \frac{54.14}{7} \Rightarrow 7.734 \text{ A} \Rightarrow I_3 = 7.734 \text{ A}$$

$$I_5 = \frac{V_2}{10} = \frac{52.22}{10} \Rightarrow I_5 = 5.222 \text{ A}$$

Soln:

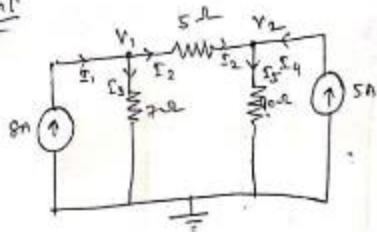

Apply KCL at node 1;

$$I_1 - I_2 - I_3 = 0$$

$$8 - \left( \frac{V_1 - V_2}{5} \right) - \frac{V_1}{7} = 0$$

$$8 - \frac{V_1}{5} + \frac{V_2}{5} - \frac{V_1}{7} = 0$$

$$-\left( \frac{1}{5} + \frac{1}{7} \right) V_1 + \frac{V_2}{5} = -8$$

$$\left( \frac{1}{5} + \frac{1}{7} \right) V_1 - \frac{V_2}{5} = 8 \rightarrow \textcircled{1}$$

Apply KCL at node 2,

$$I_2 + I_4 - I_5 = 0$$

$$\frac{V_1 - V_2}{5} + 5 - \frac{V_2}{10} = 0$$

$$\frac{V_1}{5} - \frac{V_2}{5} + 5 - \frac{V_2}{10} = 0$$

$$\frac{V_1}{5} - \left( \frac{1}{5} + \frac{1}{10} \right) V_2 = -5$$

$$-\frac{V_1}{5} + \left( \frac{1}{5} + \frac{1}{10} \right) V_2 = 5 \rightarrow \textcircled{2}$$

matrix formation,

$$\begin{bmatrix} \frac{1}{5} + \frac{1}{7} & -\frac{1}{5} \\ -\frac{1}{5} & \frac{1}{5} + \frac{1}{10} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 8 \\ 5 \end{bmatrix}$$

$$D = \begin{vmatrix} \frac{1}{5} + \frac{1}{7} & -\frac{1}{5} \\ -\frac{1}{5} & \frac{1}{5} + \frac{1}{10} \end{vmatrix} = \begin{vmatrix} \frac{12}{35} & -\frac{1}{5} \\ -\frac{1}{5} & \frac{3}{10} \end{vmatrix}$$

$$= \frac{12}{35} \left( \frac{3}{10} \right) - \left( -\frac{1}{5} \right) \left( -\frac{1}{5} \right) = \frac{36}{350} - \frac{1}{25}$$

$$D = 0.0628$$

$$\therefore D_1 = 3.4; D_2 = 3.314$$

$$V_1 = \frac{3.4}{0.0628} = 54.14 \text{ V}$$

$$V_2 = \frac{3.314}{0.0628} = 52.77 \text{ V}$$

ct: at each R,  
current thru' 5Ω;

$$I_2 = \frac{V_1 - V_2}{5} = \frac{54.14 - 52.77}{5} = 0.274 \text{ A}$$

$$I_2 = 0.274 \text{ A}$$

$$I_3 = \frac{V_1}{7} = \frac{54.14}{7} \Rightarrow 7.734 \text{ A} \Rightarrow I_3 = 7.734 \text{ A}$$

$$I_5 = \frac{V_2}{10} = \frac{52.77}{10} \Rightarrow I_5 = 5.277 \text{ A}$$