



**Chettinad**

College of Engineering & Technology

Approved by AICTE, New Delhi and Affiliated to Anna University - Chennai

**Academic Year 2023 -2024**

**Notes of Lesson**

Year/Semester: I/II

Department : ECE

Unit : III

Date: 06.03.2024

Subject Code/Title : EC3251/ Circuit Analysis

Total Hours : 60 Hrs

Faculty Name : Mrs. A. Karthikeyani

Subject Credit : 4

**Unit III: Sinusoidal Steady State Analysis**

UNIT - III - Sinusoidal Steady State Analysis

Sinusoidal steady state analysis, characterization of sinusoids, The complex forcing function, The phasor, phasor - relationship for R, L & C, Impedance and Admittance, Nodal and mesh Analysis, phasor diagrams, AC circuit power analysis, Instantaneous power, Average power, Apparent power and power factor, complex power.


A.C Fundamentals:

Sinusoidal s/s:

→ "Fundamental s/s which is used to describe a smooth periodic oscillations"   
 mathematically, it can be defined as   
 [ Vibrations ]

$$x(t) = A \sin(2\pi ft + \phi)$$

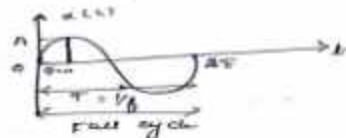where  $x(t)$  → time varying function   
 A → Amplitude   
 f → frequency (1/T)   
 φ → phase angle   
 ω = 2πf   
 Angular frequency



[ The same s/s will be repeated ]




φ → may be called as time delay.

### Applications of sine wave:

- (1) Can be used as simple building blocks to describe any periodic waveform
- (2) widely used in the field of mathematics, physics, engineering, etc.
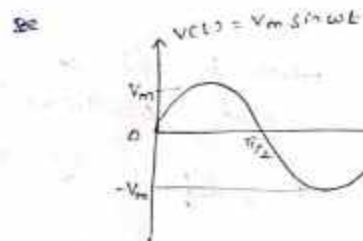
### Example:

In real time, used in GPS, tracking system, electrical appliances, cell phones, etc.



$\therefore V_{RMS} = \frac{1}{\sqrt{2}} V_m$

↓  
Peak to peak voltage

$\omega = 2\pi f = \frac{2\pi}{T}$

$f = \frac{\omega}{2\pi}$

$\therefore T = \frac{2\pi}{\omega}$

Suppose of,


$V_1(t) = V_m \sin(\omega t \pm \theta)$

$V_2(t) = V_m \sin(\omega t)$

$V_3(t) = V_m \sin(\omega t + \theta)$

$V_4(t) = V_m \sin(\omega t - \theta)$

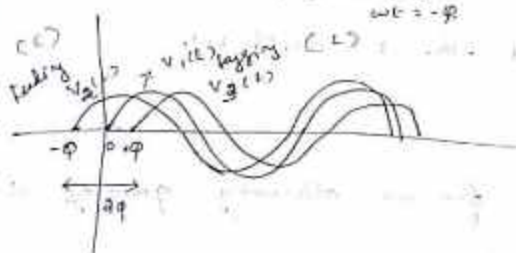$V_1(t) = V_m \sin(\omega t + \theta) = 0$   
 $\omega t = -\theta$



⇒ To compare 2 sinusoids → should have same 'f'  
" " " expression (sinusoidal)  
" " " value

### Advantages of Sinusoids:

⇒ " Note: For arithmetic operations to be performed in AC circuits, it is necessary to find magnitude and angle.

(1) Sinusoidal volt & i produce less iron and copper losses in AC rotating machines & transformers. It improves the efficiency.

(2) Sinusoidal 'v' & 'i' will offer less interference to nearby telephone lines. (unwanted)


(3) They produce less disturbance in the electrical circuits.

### Basic terms:

(i) waveform: (W/F)

" Graph drawn b/w the alternating quantity as ordinate & time"

Many types of W/F:

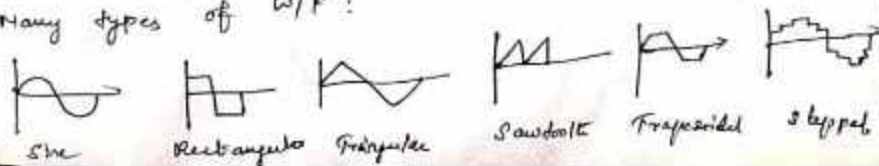

(2) cycle:

"set of +ve and -ve portions of w/f"

(3) Time period:

"Time required for an alternating quantity to complete one cycle"

1. Resistance  $\rightarrow$  oppose flow of  $e^-$  (or) current



$$R = \frac{V}{I}$$



AC  $\rightarrow$  V & I  $\rightarrow$  alternate direction  $\rightarrow$  for

Reactance:



$\Rightarrow$  when  $e^-$  flow thro' the inductor  $\rightarrow$  magnetic field will be produced

$\downarrow$   
this will generate energy  $\rightarrow$  supplied to the load

$\rightarrow$  opposes change in current


$\rightarrow$  reactance offered by 'L'  $\Rightarrow X_L$

$$X_L = 2\pi fL \text{ (ohm)}$$

f = frequency

L = Inductance

$$X_L \propto f$$

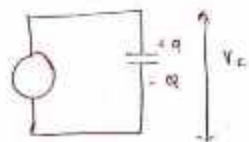


$\Rightarrow X_C \Rightarrow$  oppose sudden changes of voltage

$$X_C = \frac{1}{2\pi fC} \text{ (ohm)}$$

$$X_C \propto \frac{1}{f}$$

(R, L), (R, C), (L, C), (R, L, C)

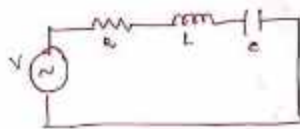

$\Rightarrow$  Impedance = [Resistance + Reactance]

$$Z = \sqrt{R^2 + X^2} \text{ ohm}$$

$$V = IZ, I = \frac{V}{Z}, Z = \frac{V}{I}$$

Phasor and phasor diagram:


Phasor:

$\Rightarrow$  Representation of a sinusoidal signal in complex number


$\Rightarrow$  in terms of polar form,  $\square^A$  form (or) vector form

Phasor diagram: (Explain the relation b/w I & V)

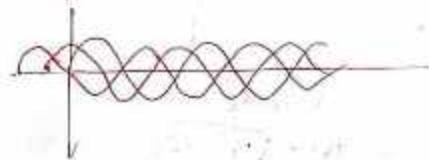
$\Rightarrow$  particularly useful when we have more than one sinusoidal signal which is having same frequency but diff amplitude & phase



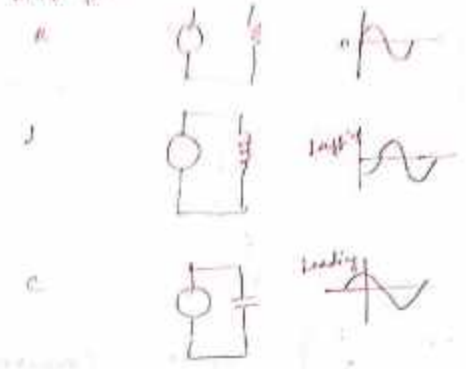
Lead type circuit  $V/I$   $\omega/L$  Vector diagram



Phase Relationship for L:

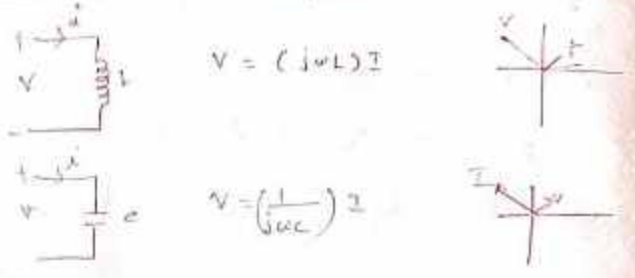

Series RL circuit phase diagram:

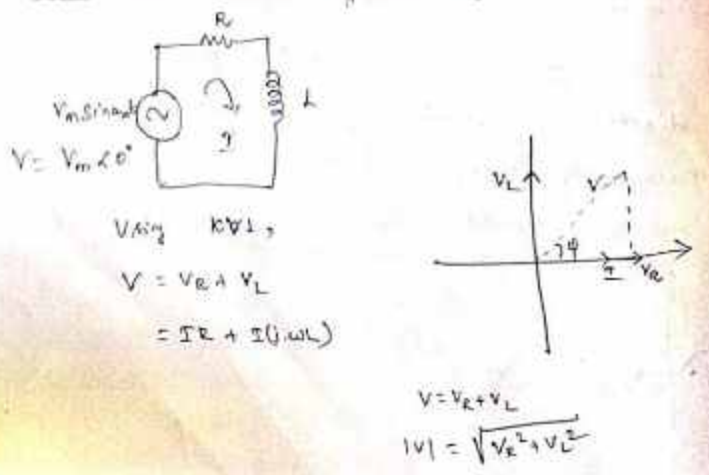

$$\phi = \tan^{-1} \left( \frac{V_L}{V_R} \right)$$


$$V(t) = V_m \sin(\omega t)$$

$$I(t) = I_m \sin(\omega t - \phi)$$





$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

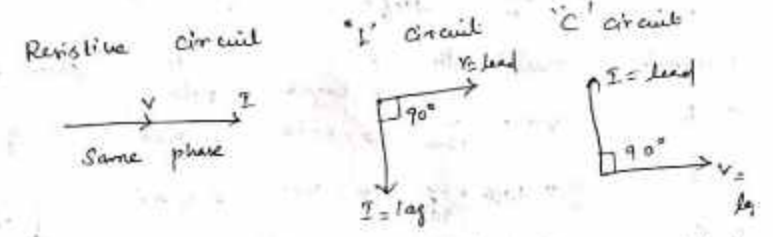$\Rightarrow$  phasor diagram direction is anticlockwise



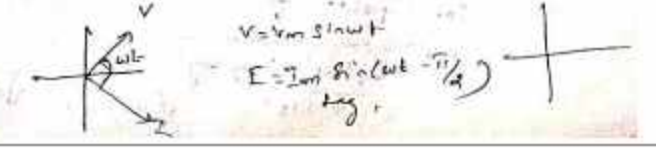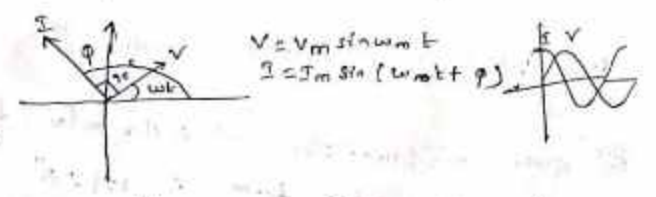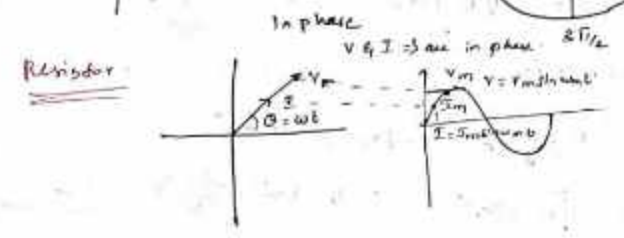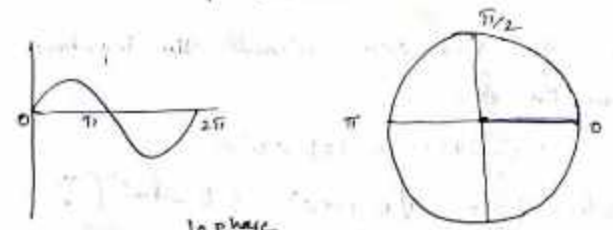Note: AC circuits  $\rightarrow$  will keep change in magnitude & direction a.r. to time



Impedance in A.C. circuit  
 → In A.C. circuit along with the R, L, & C  
 also play an important role.

$$\Rightarrow X_L = \omega L = 2\pi f L \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} \Omega$$

Parameter	Characteristic	Z in Rectangular	Z in polar	Phase diagram
Resistor (R)	V & I in phase	$Z = R + j0$	$Z = R \angle 0^\circ$	
Inductor (L)	I lags V by 90°	$Z = 0 + jX_L$	$Z = X_L \angle 90^\circ$	
Capacitor (C)	I leads V by 90°	$Z = 0 - jX_C$	$Z = X_C \angle -90^\circ$	

Then for R-L series circuit, the impedance is represented as

$$Z = R + jX_L = |Z| \angle \theta^\circ \Omega$$

where  $|Z| = \sqrt{R^2 + (X_L)^2}$  &  $\theta = \tan^{-1}\left(\frac{X_L}{R}\right)$

R-C series,

$$Z = R + jX_C = R - jX_C = |Z| \angle \theta^\circ$$

$$|Z| = \sqrt{R^2 + (X_C)^2} \quad \theta = \tan^{-1}\left(-\frac{X_C}{R}\right)$$

1. Find Let  $Z = (10 + j15)\Omega$ . Convert this into polar form.

Soln Given  $Z = (10 + j15)\Omega \rightarrow$  Rectangular form.

For polar form  $\Rightarrow |Z| \angle \theta^\circ$

$$|Z| = \sqrt{\text{Real}^2 + \text{Imaginary}^2} \\ = \sqrt{10^2 + 15^2} = \sqrt{100 + 225} = \sqrt{325} = 18.03 \Omega$$

$$\theta = \tan^{-1}\left(\frac{\text{Imaginary}}{\text{Real}}\right)$$

$$= \tan^{-1}\left(\frac{15}{10}\right)$$

$$= 56.31^\circ$$

$$\therefore Z = 18.03 \angle 56.31^\circ$$

2. Convert  $20 - j15$  into

polar form.

$$\text{Ans: } Z = 25 \angle -36.9^\circ$$

polar form to Rectangular form:

$$Z = |Z| \angle \theta^\circ \Rightarrow Z = |Z| \cos \theta + j |Z| \sin \theta$$

$$Z = 10 \cos 60^\circ + j$$

$$Z = r \cos \phi + j r \sin \phi \\ = 12 \cos 60^\circ + j (12) \sin 60^\circ \\ X = r \cos \phi$$

$$= 10 \times \cos(60^\circ) + j (10 \times \sin(60^\circ))$$

3. Convert  $Z = 10 \angle 60^\circ$  into rectangular form:

$$r = 10; \theta = 60^\circ$$

(or)

$$|Z| = 10; \theta = 60^\circ$$

$$\Rightarrow Z = |Z| \cos \theta$$

$$= 10 \times \cos(60^\circ) = 10 \times \frac{1}{2} = 5$$

Calculator:

→ Type Real part

Shift → [R] → [P]

Enter Imaginary part

Press = (∴ shows result)

Press x → θ

↓ shows the angle

R to P:

$$X + jy = Z \angle \theta$$

$$Z = \sqrt{X^2 + Y^2}$$

$$\theta = \tan^{-1}\left(\frac{Y}{X}\right)$$

P to R:

$$Z \angle \theta = X + jy$$

$$X = r \cos \theta = r \cos \theta$$

$$Y = r \sin \theta = r \sin \theta$$

$$\sin \theta \quad 0 \quad \frac{1}{2} \quad \frac{\sqrt{2}}{2} \quad \frac{3}{4} \quad 1$$

$$\cos \theta \quad 1 \quad \frac{\sqrt{3}}{2} \quad \frac{\sqrt{2}}{2} \quad \frac{1}{2} \quad 0$$

Imaginary part:

$$\begin{aligned} y &= r \sin \theta = 12.1 \sin 5 \\ &= 10 \sin(60) \\ &= 8.66 \end{aligned}$$

$$z = 5 + j8.66 \Omega$$

Convert  $Z = 30 \angle 45^\circ$  into rectangular form  $x \rightarrow y$

Calc:

$$30 \rightarrow \text{shift} \rightarrow \text{P} \rightarrow \text{R} \rightarrow +5^\circ \rightarrow -/+ \rightarrow =$$

$$\rightarrow -21.22 \leftarrow \text{X} \rightarrow \text{Y} \leftarrow \begin{matrix} \text{d.d.} \\ \text{(Active} \\ \text{part)} \end{matrix}$$

5)  $Z_1 = 10 + j10$ ,  $Z_2 = 20 - j30$  are in series. Find  $Z_T$  in polar form

$$\begin{aligned} Z_T &= Z_1 + Z_2 = 10 + j10 + 20 - j30 \\ &= 30 - j20 \end{aligned}$$

$$Z_T = 36.1 \angle -33.7^\circ$$

6) The total impedance of a circuit in which  $Z_1$  &  $Z_2$  are in series is equal to  $(30 + j40) \Omega$ ,  $Z_1 = (20 + j60) \Omega$ . Find  $Z_2$

$$Z_T = Z_1 + Z_2$$

$$\begin{aligned} Z_2 &= Z_T - Z_1 \\ &= 30 + j40 - 20 - j60 \end{aligned}$$

$$= (10 - j20) \Omega \quad \text{Rec. form}$$

$$\Rightarrow \text{polar form} \rightarrow Z_2 = 22.36 \angle -63.42^\circ$$

Calculator:

Enter 12)

press  $\text{shift} \rightarrow \text{P} \rightarrow \text{R}$

Enter angle (8)

$\downarrow$   
-/+

$\downarrow$   
 $\rightarrow$  Active part

7) In a given circuit  $Z_1 = 10 \angle 60^\circ$ ,  $Z_2 = 20 \angle 70^\circ$  Find  $V$

$$\begin{aligned} V &= I \cdot Z = 10 \angle 60^\circ (20 \angle 30^\circ) \\ &= 200 \angle (60 + 30) \\ &= 200 \angle 90^\circ \end{aligned}$$

8) In a circuit  $V = 200 \text{ Volts}$ ;  $I = 10 \angle 30^\circ$ . Find  $Z$  both in polar & rectangular form.

$$I = \frac{V}{Z} \Rightarrow Z = \frac{V}{I} = \frac{200 \angle 0^\circ}{10 \angle 30^\circ} = 20 \angle 0^\circ - 30^\circ = 20 \angle -30^\circ$$

Problems: on Vrms:

9) Write the polar form of the voltage given by,  $V = 100 \sin(100\pi t + \pi/6) \text{ V}$ . Obtain its rectangular form.

$$\text{Given, } V_m = 100, \phi = \pi/6; V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{100}{1.414} = 70.7106 \text{ V}$$

$\therefore$  In polar form,  $70.7106 \angle 30^\circ \text{ V}$

Rectangular form,  $61.2371 + j35.3553 \text{ V}$

10) Two a.c voltages are represented by:  $V_1(t) = 30 \sin(314t + \pi/4)$   $V_2(t) = 60 \sin(314t + \pi/6)$ . Calculate the resultant voltage  $V(t)$  & express in the form of  $V(t) = V_m \sin(314t + \phi)$

$$\text{Given, } V_{m1} = 30, V_{m2} = 60$$

$$V_{rms1} = \frac{30}{\sqrt{2}}; V_{rms2} = \frac{60}{\sqrt{2}}$$

$$V_1 = \frac{30}{\sqrt{2}} \angle 45^\circ; V_2 = \frac{60}{\sqrt{2}} \angle 60^\circ$$

$$= 15 + j15 \text{ V}$$

$$V_2 = 21.2132 + j36.7433 \text{ V}$$

For addition,  $\square$  coordinates

$$V_R = V_1 + V_2$$

$$= 63.1558 \angle 55^\circ$$


$$V_{R(\text{rms})} = \sqrt{2} \times V_{\text{rms}}$$

$$= \sqrt{2} \times 63.1558$$


$$= 89.3159$$

The resultant voltage is,
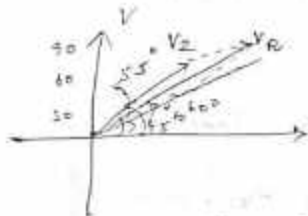
$$V(t) = 89.3159 \sin(314t + 55^\circ) \text{ V}$$



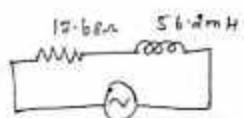(ii) Find the impedance of the circuit shown in figure.



$$V(t) = V_m \sin 314t$$

$$Z = R + jX_L$$

$$X_L = \omega L = 2\pi fL = 2\pi \times 50 \times 314 \times 56.2 \times 10^{-3}$$


$$= 17.6 \Omega$$

$$\therefore Z = R + jX_L = 17.6 \Omega + j17.6 \Omega$$

Note: The voltage will be represented in terms of  $V_{\text{rms}}$

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$$

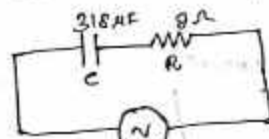(1st) Find the current in the circuit shown in figure and draw the phasor diagram.



$$V(t) = 100\sqrt{2} \sin 314t$$

Given,  $C = 318 \mu\text{F}$ ,  $R = 8 \Omega$ ,  $V_m = 100\sqrt{2}$ ,  $2\pi f = 314 \text{ rad/s}$

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}} = \frac{100\sqrt{2}}{\sqrt{2}} = 100 \text{ V} \text{ \& phase} = 0^\circ \Rightarrow$$

$$V_{\text{rms}} = 100 \angle 0^\circ \text{ V}$$


$$X_C = \frac{1}{2\pi f C} = \frac{1}{314 \times 318 \times 10^{-6}} = 10 \Omega$$

$$\therefore Z = R - jX_C$$


$$Z = 8 - j10$$

$$\therefore I = \frac{V}{Z} = \frac{100 \angle 0^\circ}{12.806 \angle -51.34^\circ}$$

$$I = 7.808 \angle 51.34^\circ$$

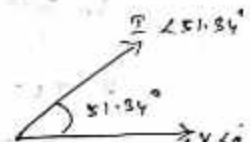


Series R-L-C circuit.

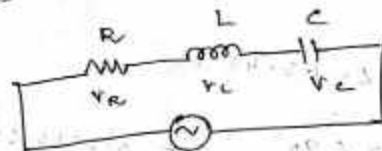

$$\therefore Z = R + jX_L - jX_C$$

$$= R + j(X_L - X_C)$$

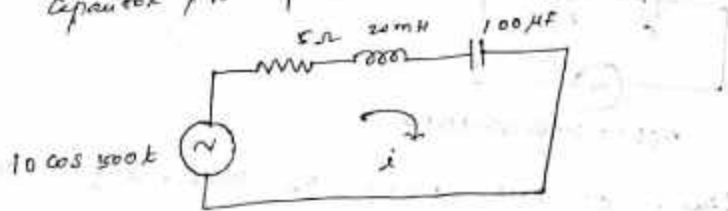13. The network shown in figure is operating in a sinusoidal steady state. Find  $V$  across capacitor,  $R$  &  $L$ .



$$V \angle \theta = 10 \cos 500t = 10 \sin(500t + 90^\circ) \quad [\because \sin(90 + \theta) = \cos \theta]$$

$$R = 5 \quad \therefore \theta = 90^\circ$$

$$L = 20 \text{ mH}$$

$$C = 100 \mu\text{F}$$

$$\omega = 500 = \text{rad/s}$$

$$V_m = 10 \Rightarrow V_{\text{rms}} = \frac{10}{\sqrt{2}} \angle 90^\circ = 7.071 \text{ V} \angle 90^\circ$$

$$X_L = \omega L = 500 \times 20 \times 10^{-3} = 10 \Omega$$

$$X_C = \frac{1}{\omega C} = 20 \Omega$$

$$\therefore X_T = 5 + j(10 - 20)$$

$$= 5 - j10 \Omega$$

$$R_T = 11.1803 \angle -63.43^\circ \Omega$$

$$i = \frac{V}{R_T} = \frac{7.07 \angle 90^\circ}{11.1803 \angle -63.43^\circ} = 0.6324 \angle 153.43^\circ \text{ A}$$

$$\therefore V_R = 0.6324 \angle 153.43^\circ \times 5$$

$$V_R = 0.6324 \times 5 = 3.162 \text{ V}$$

$$V_L = 0.6324 \times X_L = 0.6324 \times 10 = 6.324 \text{ V}$$

$$V_C = 0.6324 \times X_C = 0.6324 \times 20 = 12.648 \text{ V}$$

Admittance: (A.C parallel circuit)

$$Y = \frac{1}{Z}$$


$$Y = G + jB$$

$G \rightarrow$  Conductance

$B \rightarrow$  Susceptance


Loop Analysis (or) Mesh Analysis:

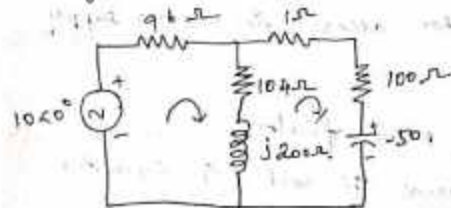14. Find the current through the source and capacitor in the network shown below, using mesh current analysis.



Step 1:

Show the mesh currents

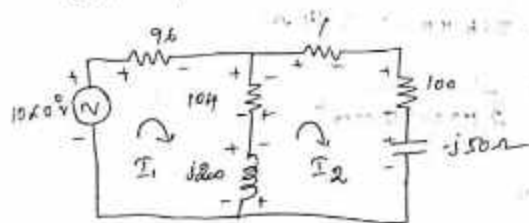

Step 2: Apply KVL to the two loops.

$$-10 \angle 0^\circ + 9I_1 + 10I_1 + j20I_1 - 10I_2 - j20I_2 = 0$$

$$200I_1 + j200I_1 - (104 + j200)I_2 = 10 \angle 0^\circ$$

$$\Rightarrow (200 + j200)I_1 - (104 + j200)I_2 = 10 \angle 0^\circ \rightarrow (1)$$



$$\begin{aligned} (205 + j150)I_1 - (104 + j200)I_2 &= 0 \\ \Rightarrow \begin{vmatrix} 205 + j150 & -104 + j200 \\ -104 + j200 & 205 + j150 \end{vmatrix} \end{aligned}$$

$$\therefore \Delta = (205 + j150)(205 + j150) - (-104 + j200)(-104 + j200)$$

$$\therefore I_1 = 0.05101 \angle 20^\circ \text{ A}$$

$$I_2 = 0.04587 \angle 26.335^\circ \text{ A}$$

Part C - May/June 2022

15) A coil of  $R=10\Omega$ ,  $L=0.1\text{H}$  is connected in series with  $150\mu\text{F}$  capacitor across  $200\text{V}$ ,  $50\text{Hz}$  supply.

Calculate,

(i)  $X_L$ ,  $X_C$ ,  $Z$ ,  $I$  & power factor

(ii) The voltage across the coil & capacitor.

Solution:

$$\begin{aligned} X_L &= 2\pi fL = 2\pi \times 50 \times 0.1 \\ &= 31.4 \times 0.1 = 3.14\Omega \end{aligned}$$

$$\begin{aligned} X_C &= \frac{1}{2\pi fC} = \frac{1}{2\pi \times 50 \times 150 \times 10^{-6}} \\ &= 81.23\Omega \end{aligned}$$

$$Z = R + jX_L - jX_C$$

$$= 10 - j18.09\Omega$$

$$I = \frac{200}{10 - j18.09} = \frac{200 \angle 0^\circ}{20.67 \angle -61.068^\circ}$$

$$\Rightarrow I = 9.675 \angle 61.068^\circ$$


$$\phi = 61.068^\circ$$

$$\begin{aligned} \rightarrow \text{power factor} &= \cos \phi \\ &= \cos(61.068^\circ) \\ &= 0.4838 \end{aligned}$$

(ii)

$$V_L = 9.675 \times 3.14 = 30.3995\text{V}$$
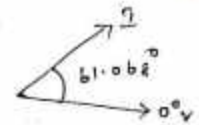
$$V_C = 9.675 \times 81.23 = 785.4003\text{V}$$



May/June (April/May-2022) (or)

16) A resistance of  $100\Omega$  is connected in series with a  $50\mu\text{F}$  capacitor. When the supply voltage is  $200\text{V}$ ,  $50\text{Hz}$ . Find the

(i) Impedance, current & power factor

(ii) The voltage across the resistor & across capacitor. Draw the phasor diagram.

Solution:

Given:

$$R = 100\Omega, C = 50\mu\text{F}, V = 200\text{V} = 200 \angle 0^\circ$$

$$f = 50\text{Hz}$$

$$(i) Z = R + (-jX_C) = R - jX_C$$

$$\begin{aligned} X_C &= \frac{1}{\omega C} = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 50 \times 10^{-6}} \\ &= 63.69\Omega \end{aligned}$$

$$\therefore Z = 100 - j63.69\Omega$$


$$I = \frac{V}{Z} = \frac{200 \angle 0^\circ}{100 - j63.69}$$

$$|Z| = \sqrt{100^2 + 63.69^2} = 118.56 \angle -32.49^\circ$$

$$\therefore I = 1.69 \angle 32.49^\circ \text{ A}$$

$$V = 200 \angle 0^\circ ; I = 1.69 \angle 32.49^\circ$$
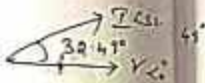
$$\text{power factor} = \cos \phi = \cos(32.49^\circ) = 0.8435$$




$$V_R = 1.69 \times 100 = 169 \text{ Volts}$$

$$V_C = 1.69 \times 50 \times 10^{-4} = 84.5 \mu\text{V} \rightarrow (0.0845 \text{ mV})$$

### Loop Analysis (or) Mesh Analysis

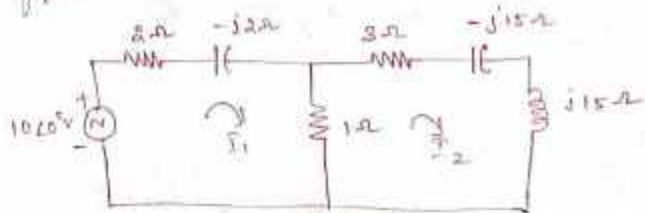- (17) Apply mesh current method and determine currents through the resistors of the network shown in figure.



Soln:

Apply KVL to loop 1

$$-10 \angle 0^\circ + (2 - j2)I_1 - I_2 = 0$$

$$\Rightarrow (3 - j2)I_1 - I_2 = 10 \angle 0^\circ$$

Apply KVL to loop 2

$$-I_1 + (3 + j0)I_2 = 0$$

$$-I_1 + 3I_2 = 0$$

In matrix,

$$\begin{bmatrix} 3 - j2 & -1 \\ -1 & 3 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 10 \angle 0^\circ \\ 0 \end{bmatrix}$$

$$\Delta = 11 - j8 = 13.6 \angle -36^\circ$$

$$\Delta_1 = 40 \angle 0^\circ ; \Delta_2 = 10 \angle 0^\circ$$

$$\therefore I_1 = \frac{\Delta_1}{\Delta} = \frac{40 \angle 0^\circ}{13.6 \angle -36^\circ} = 2.94 \angle 36^\circ \text{ A}$$


$$I_2 = \frac{\Delta_2}{\Delta} = \frac{10 \angle 0^\circ}{13.6 \angle -36^\circ} = 0.735 \angle 36^\circ \text{ A}$$

$$\begin{aligned} (I_1 - I_2) &= (2.94 \angle 36^\circ - 0.735 \angle 36^\circ) \\ &= 2.205 \angle 36^\circ \\ &= 2.205 \angle 36^\circ \end{aligned}$$

$$\begin{aligned} \therefore I_1 &= 2.94 \angle 36^\circ \\ I_2 &= 0.735 \angle 36^\circ \\ I_1 - I_2 &= 2.205 \angle 36^\circ \end{aligned}$$

~~\therefore The current through 2Ω = 2.205 ∠ 36°~~

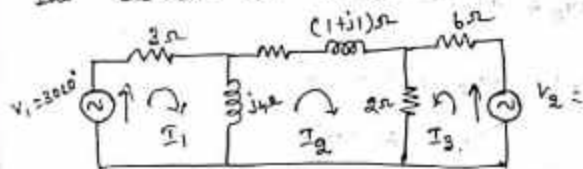- (18) In the network shown in figure, find  $V_2$  such that the current in the  $(1+j1)\Omega$  branch is zero.



Solution:

The directions of all loop currents are already given in the problem. Without changing the directions, the problem is solved:

Given that the current thru,

$$(1+j)I_2 = 0$$

$$\Rightarrow I_2 = \frac{0}{1+j} = 0$$

$$\Rightarrow \boxed{D_2 = 0}$$

In the matrix form, we get the loop equations as below:

$$\begin{bmatrix} 3+j4 & -j4 & 0 \\ -j4 & 3+j5 & +2 \\ 0 & 2 & 8 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 30 \angle 0^\circ \\ 0 \\ V_2 \end{bmatrix}$$

$$\therefore D_2 = \begin{vmatrix} 30 \angle 0^\circ & 30 \angle 0^\circ & 0 \\ -j4 & 0 & 2 \\ 0 & V_2 & 8 \end{vmatrix} = 0$$

$$(3+j4)(-2V_2) - 30 \angle 0^\circ (-j32) = 0$$

$$-5.45^\circ \times 2V_2 + 960 \angle 90^\circ = 0$$


$$1.0253^\circ \times V_2 = 1960 \angle 90^\circ$$

$$V_2 = 1960 \angle 90^\circ$$

$$10.253^\circ$$

$$\boxed{V_2 = 91 \angle 37^\circ \text{ Volts}}$$

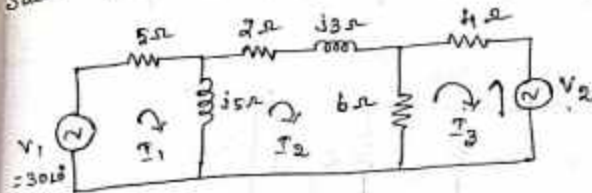19) In the network shown in figure determine  $V_2$  such that the current in  $2+j3$  impedance is zero.



Solution:

In the third loop, the current is in clockwise direction.

Given that,

The current thru'  $(2+j3)$  is zero.

∴

$$I_2 = 0$$

$$\Rightarrow I_2 = \frac{0}{2+j3} = 0$$

$$\begin{bmatrix} 5+j5 & -j5 & 0 \\ -j5 & 8+j8 & -6 \\ 0 & -6 & 10 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 30 \angle 0^\circ \\ 0 \\ -V_2 \end{bmatrix}$$

$$D_2 = \begin{vmatrix} 5+j5 & 30 \angle 0^\circ & 0 \\ -j5 & 0 & -6 \\ 0 & -V_2 & 10 \end{vmatrix} = 0$$


$$\Rightarrow (5+j5)(-6V_2) - 30 \angle 0^\circ (-j50) = 0$$

$$(-30 - j30)V_2 + 1500j = 0$$

$$V_2 = \frac{1500j}{30 + j30} = \frac{500j}{1+j1}$$

$$= 25 + 25j = 35.36 \angle 45^\circ$$

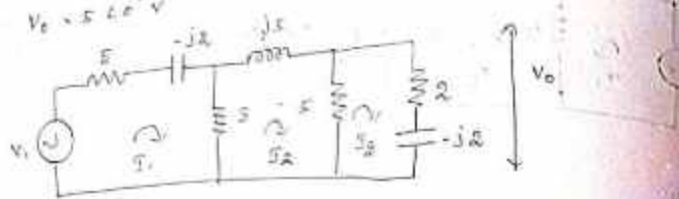Q2) In the circuit shown in figure the source  $V_1$  results in a voltage  $V_0$  across the  $(2-j2)\Omega$  impedance. Find the source  $V_1$  which corresponds to  $V_0 = 5 \angle 20^\circ \text{ V}$ .



Given;  $V_0 = 5 \angle 20^\circ$

$$I_2 = \frac{V_0}{2-j2} = \frac{5 \angle 20^\circ}{2.832 \angle -45^\circ} = 1.77 \angle 45^\circ \text{ A}$$

$$\begin{bmatrix} R-j2 & -2 & 0 \\ -2 & 2+j2 & -2 \\ 0 & -2 & 2-j2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ 0 \\ 0 \end{bmatrix}$$

$$\Delta = 504 \angle 4.32^\circ$$

$$I_2 = V_1(15)$$

$$I_2 = \frac{I_2}{\Delta} = \frac{V_1(15)}{504 \angle 4.32^\circ}$$

$$= 1.77 \angle 45^\circ$$

$$V_1 = 59.5 \angle 45.32^\circ \text{ V}$$

### Nodal Analysis Method:

**Node:** It is a point where two or more circuit elements terminals are connected together.

**Branch:** The connection between nodes.

### Steps to Analyze AC Circuits


1. Transform the circuit to the phasor or frequency domain.

2. Solve the problem using circuit techniques.

3. Transform the resulting phasor to the time domain.



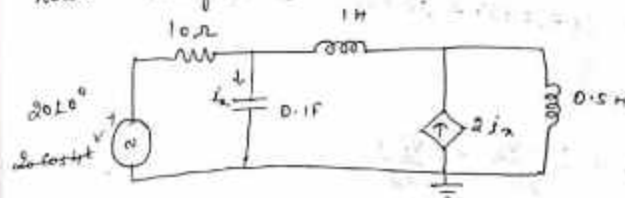Q3) Find  $i_x$  in the circuit of figure using nodal analysis.  $\omega = 4 \text{ rad/s}$ .




### Solution:

Given  $\omega = 4$

$$\Rightarrow \text{So } 1H = j\omega L = j4$$

$$0.5H = j\omega L = j2$$
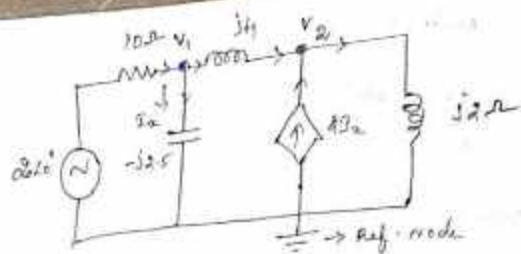
$$0.1F = \frac{1}{j\omega C} = \frac{1}{j(4)(0.1)} = \frac{1}{j(0.4)} = -j2.5$$



At Node 1, KCL

$$\frac{20 - V_1}{10} = \frac{V_1 - 0}{-j2.5} + \frac{V_1 - V_2}{j4}$$

$$20 - V_1 = \frac{10V_1}{-j2.5} + \frac{10(V_1 - V_2)}{j4}$$

$$= \frac{4V_1}{-j} + \frac{2.5(V_1 - V_2)}{j}$$

$$j2.5V_1 = 4jV_1 - 2.5(V_1 - V_2)$$

~~20 =~~

$$20 = V_1 + j4V_1 - 2.5jV_1 + 2.5jV_2$$

$$20 = (1 + j1.5)V_1 + j2.5V_2 \rightarrow \textcircled{1}$$

At Node 2, KCL,

$$2I_x + \frac{V_1 - V_2}{j4} = \frac{V_2 - 0}{j2}$$

$$I_x = \frac{V_1}{-j2.5} \Rightarrow 2 \left( \frac{V_1}{-j2.5} \right) + \frac{V_1 - V_2}{j4} = \frac{V_2}{j2}$$

$$j0.8V_1 + j0.25V_1 + j0.25V_2 = -j0.5V_2$$

$$j0.65V_1 + j0.25V_2 = 0 \rightarrow \textcircled{2}$$

$$\begin{bmatrix} 1 + j1.5 & j2.5 \\ j0.65 & j0.75 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 0 \end{bmatrix}$$

$$D = \begin{vmatrix} 1 + j1.5 & j2.5 \\ j0.65 & j0.75 \end{vmatrix}$$

$$= (1 + j1.5)(j0.75) - j2.5(j0.65)$$

$$= 0.5 + 0.75j$$

$$D_1 = \begin{vmatrix} 20 & j2.5 \\ 0 & j0.75 \end{vmatrix} = 15$$


$$\therefore V_1 = \frac{15}{0.5 + 0.75j} = 16.4 \angle -56^\circ$$

$$V_2 = 13.91 \angle 192.5^\circ \text{ V}$$

$$I_x = \frac{V_1}{j2.5} = 4.29 \angle 100.5^\circ \text{ A}$$

Solve:

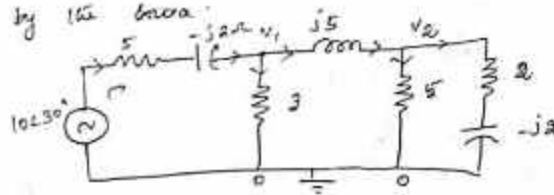Q1) In the network shown in figure, find the node voltages  $V_1$  &  $V_2$ . Find also the current supplied by the source.



$$\frac{20 \angle 30^\circ - V_1}{5 - j2} = \frac{V_1}{3} + \frac{V_1 - V_2}{j5}$$


$$\frac{20 \angle 30^\circ - V_1}{5 - j2} = \frac{V_1}{3} + \frac{V_1 - V_2}{j5}$$

$$\frac{20 \angle 30^\circ}{5 - j2} = \frac{V_1}{5 - j2} + \frac{V_1}{3} + \frac{V_1 - V_2}{j5}$$

$$V_1 \left( \frac{1}{5 - j2} + \frac{1}{3} + \frac{1}{j5} \right) - \frac{1}{j5} V_2 = \frac{8.66 + j5}{5 - j2}$$

$$V_1 \left( \frac{1}{5 - j2} + \frac{1}{3} + \frac{1}{j5} \right) - \frac{1}{j5} V_2 = 1.86 \angle 51.8^\circ \quad \text{--- (1)}$$

Apply KCL at node 2,

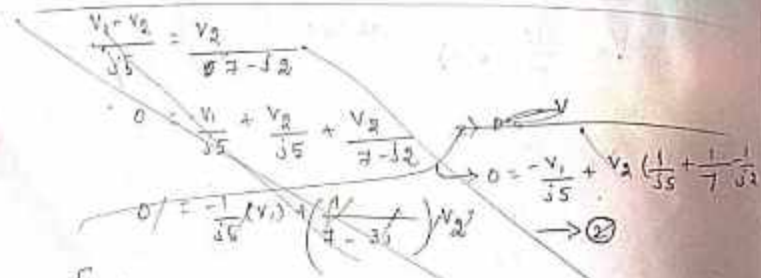

$$\left[ \begin{array}{cc} \frac{1}{5 - j2} + \frac{1}{3} + \frac{1}{j5} & -\frac{1}{j5} \\ -\frac{1}{j5} & \frac{1}{5} \end{array} \right] \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 1.86 \angle 51.8^\circ \\ 0 \end{bmatrix}$$

$$\frac{V_1 - V_2}{j5} = \frac{V_2}{5} + \frac{V_2}{2 - j2}$$

$$\frac{V_1}{j5} - \frac{V_2}{j5} = \frac{V_2}{5} + \frac{V_2}{2 - j2}$$

$$0 = \frac{-V_1}{j5} + V_2 \left( \frac{1}{j5} + \frac{1}{5} + \frac{1}{2 - j2} \right) \quad \text{--- (2)}$$

$$\left[ \begin{array}{cc} \frac{1}{5 - j2} + \frac{1}{3} + \frac{1}{j5} & -\frac{1}{j5} \\ -\frac{1}{j5} & \frac{1}{5} + \frac{1}{5} + \frac{1}{2 - j2} \end{array} \right] \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 1.86 \angle 51.8^\circ \\ 0 \end{bmatrix}$$

$\Delta = \det(A)$

$$\begin{bmatrix} 0.51 - j0.13 & j0.2 \\ j0.2 & 0.45 + j0.05 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 1.86 \angle 51.8^\circ \\ 0 \end{bmatrix}$$

$$\Delta = (0.51 - j0.13)(0.45 + j0.05) - j^2 0.04$$

$$= 0.276 - j0.033 = 0.278 \angle -6.82^\circ$$

$$\Delta_1 = \begin{vmatrix} 1.86 \angle 51.8^\circ & j0.2 \\ 0 & 0.45 + j0.05 \end{vmatrix}$$

$$= (1.86 \angle 51.8^\circ)(0.45 + j0.05)$$

$$= (1.86 \angle 51.8^\circ)(0.453 \angle 6.3^\circ)$$

$$\Delta_1 = 0.843 \angle 58.1^\circ$$

$$\Delta_2 = (-j0.2)(1.86 \angle 51.8^\circ)$$

$$= (0.2 \angle -90^\circ)(1.86 \angle 51.8^\circ)$$

$$= 0.372 \angle -38.2^\circ$$

$$\therefore V_1 = \frac{\Delta_1}{\Delta} = \frac{0.843 \angle 58.1^\circ}{0.278 \angle -6.82^\circ}$$

$$V_1 = 3.03 \angle 64.9^\circ \text{ V}$$

Similarly,

$$V_2 = 1.34 \angle -31.38^\circ \text{ V}$$

From the given fig. 2 current supplied by source,


$$\frac{10 \angle 30^\circ - V_1}{5 - j2} = \frac{10 \angle 30^\circ - 5.03 \angle 64.9^\circ}{5 - j2}$$

$$= \frac{(8.66 + j5) - (1.3 + j2.75)}{5.29 \angle -21.8^\circ}$$

$$= \frac{7.36 - j2.25}{5.29 \angle -21.8^\circ} = \frac{7.7 \angle -17^\circ}{5.29 \angle -21.8^\circ}$$

$$= \underline{1.43 \angle 4.8^\circ \text{ A}}$$

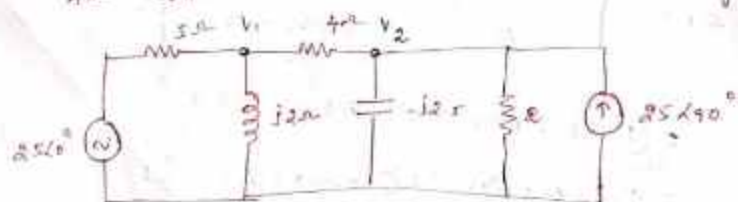Q24 Using nodal analysis, find the current through 4Ω resistor in the circuit shown in figure



Formula:

$$\begin{bmatrix} \frac{1}{R_A} + \frac{1}{R_B} + \frac{1}{R_C} & -\frac{1}{R_B} \\ -\frac{1}{R_B} & \frac{1}{R_B} + \frac{1}{R_C} + \frac{1}{R_D} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \frac{V_1}{R_A} \\ \frac{V_2}{R_B} \end{bmatrix}$$

$$\begin{bmatrix} \frac{1}{5} + \frac{1}{j2} + \frac{1}{4} & -\frac{1}{4} \\ -\frac{1}{4} & \frac{1}{4} + \frac{1}{j2.5} + \frac{1}{2} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \frac{25 \angle 90^\circ}{5} \\ \frac{25 \angle 90^\circ}{4} \end{bmatrix}$$

$$D = 0.513 \angle -21.3^\circ$$

$$D_1 = 9.06 \angle 65.5^\circ$$

$$D_2 = 14.77 \angle 39.3^\circ$$

$$\therefore V_1 = 17.64 \angle 87.8^\circ \text{ V} = (0.677 + j17.6) \text{ V}$$

$$V_2 = 34.64 \angle 61.6^\circ \text{ V} = (16.47 + j30.47) \text{ V}$$

$$\therefore \text{V across } 4\Omega = V_1 - V_2 = V_2 - V_1$$


$$= 15.793 + j12.87$$

$$= 20.37 \angle 39.17^\circ \text{ V}$$

$$\therefore \text{I through } 4\Omega = \frac{20.37 \angle 39.17^\circ}{4}$$

$$= \underline{5.0925 \angle 39.17^\circ \text{ A}}$$

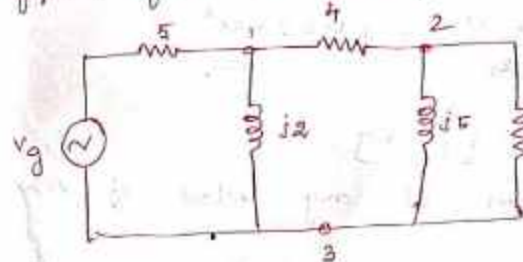Q25 Given the nodes 1 & 2 in network of figure, find the ratio of node voltage  $V_1/V_2$ .



Solution:

$$\begin{bmatrix} \frac{1}{5} + \frac{1}{j2} + \frac{1}{4} & -\frac{1}{4} \\ -\frac{1}{4} & \frac{1}{4} + \frac{1}{j5} + \frac{1}{10} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \frac{V_g}{5} \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} 0.45 + j0.5 & -0.25 \\ -0.25 & 0.35 + j0.2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 0.2V_g \\ 0 \end{bmatrix}$$

$$\Delta_1 = \begin{vmatrix} 0.2V_g & -1.2R \\ 0 & 0.35-j2 \end{vmatrix}$$

$$= 0.2V_g(0.35-j2.2)$$

$$\Delta_2 = \begin{vmatrix} 0.45-j0.5 & 0.2V_g \\ -0.2R & 0 \end{vmatrix}$$

$$= 0.2V_g(0.25) = 0.05V_g$$

$$V_1 = \frac{\Delta_1}{\Delta} \quad ; \quad V_2 = \frac{\Delta_2}{\Delta} \Rightarrow \frac{V_1}{V_2} = \frac{\Delta_1/\Delta_2}{0.25/0.25} = \frac{\Delta_1}{\Delta_2}$$

$$\Rightarrow \frac{V_1}{V_2} = \frac{0.2V_g(0.35-j2.2)}{0.05V_g}$$

$$= \frac{0.35-j2.2}{0.25} = 1.4 - j8.8$$

Instantaneous Power: [P(t)]

"The electric power at any instant of time"

$\Rightarrow$  watts

$\Rightarrow P(t) = \text{Instantaneous } V' (v(t)) \times \text{Instantaneous } I' (i(t))$

$\downarrow$

By an element

$$P(t) = v(t) \times i(t)$$

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

$$\therefore P(t) = V_m \cos(\omega t + \theta_v) \times I_m \cos(\omega t + \theta_i)$$

$$= V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$

$$\therefore \cos A \cos B = \frac{\cos(A-B) + \cos(A+B)}{2}$$

$$\therefore = \frac{V_m I_m}{2} [\cos(\omega t - \theta_v + \theta_i) + \cos(2\omega t + \theta_v + \theta_i)]$$

$$= \frac{V_m I_m}{2} [\cos(\theta_v - \theta_i) + \cos(2\omega t + \theta_v + \theta_i)]$$

Inst. Power:

$$P(t) = \underbrace{\frac{V_m I_m}{2} \cos(\theta_v - \theta_i)}_{\text{Time independent term}} + \underbrace{\frac{V_m I_m}{2} \cos(2\omega t + \theta_v + \theta_i)}_{\text{Time dependent term}}$$

Note: P(t) is dependent on time difficult to measure time P(t)

Average Power: [Time independent] [P<sub>av</sub>]

"Average of instantaneous power over one period"

$$P_{av} = \frac{1}{T} \int_{t_1}^{t_2} P(t) dt$$

$$t \rightarrow \omega t$$

$$t = 0 \Rightarrow 0$$

$$t = T \Rightarrow \frac{2\pi}{\omega} \times \omega T = 2\pi$$

(or)

$$P_{av} = \frac{1}{2\pi} \int_0^{2\pi} P(t) dt$$

$$\rightarrow P_{av} = \frac{1}{T} \int_0^T \left[ \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i) \right] dt$$

$$= \frac{1}{T} \times \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \int_0^T dt + \frac{1}{T} \times \frac{1}{2} V_m I_m \int_0^T \cos(2\omega t + \theta_v + \theta_i) dt$$

$\int_0^T \cos(2\omega t + \theta_v + \theta_i) dt = 0$   
Sine wave for one period



$$= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \left( \frac{1}{T} \times T \right) + 0$$

$$\Rightarrow P_{av} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$\text{or}$$

$$= \frac{1}{2} V_m I_m [\cos(\theta_i - \theta_v)]$$

$$= \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \cos(\theta_v - \theta_i)$$

$$P_{av} = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

**Case 1** if  $\theta_v = \theta_i$ : [Both  $V$  &  $I$  are in same phase]

$$P_{av} = V_{rms} I_{rms} \cos(0^\circ)$$

$$P_{av} = V_{rms} I_{rms}$$

or

$$P_{av} = \frac{1}{2} I_m R \cdot I_m = \frac{1}{2} I_m^2 R \quad [\text{in } R, \theta_v = \theta_i]$$

**Case 2:**

$$\text{if } \theta_v - \theta_i = \pm 90^\circ \quad [\cos 90^\circ \text{ \& } \cos(-90^\circ) = 0]$$

$P_{av} = 0 \Rightarrow$  purely reactive circuit

Note: The  $R$  will absorb the power all the

time &  $L$  &  $C$  absorb zero Avg. power

$$\vec{V} \text{ in phase} = V_m \angle \theta_v$$

$$\vec{I} \text{ " } = I_m \angle \theta_i$$

$$\vec{I}^* = I_m \angle -\theta_i$$

$$\vec{V} \cdot \vec{I}^* = V_m I_m \angle (\theta_v - \theta_i)$$

$$= V_m I_m [\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i)]$$


$$\therefore \text{Re} \{ \vec{V} \cdot \vec{I}^* \} = V_m I_m \cos(\theta_v - \theta_i)$$

$$\vec{V} \cdot \vec{I}^* = V_m I_m \angle (\theta_v - \theta_i)$$

$$= V_m I_m [\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i)]$$

$$\frac{1}{2} \text{Re} \{ \vec{V} \cdot \vec{I}^* \} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = P_{av}$$

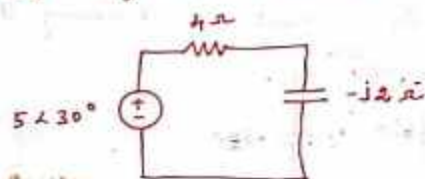**Q4** For the circuit shown, find the average power supplied by the source and the average power absorbed by the resistor.



Solution:

$$P_{av} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$V_m = ? ; I_m = ? ; \theta_v = ? ; \theta_i = ?$$

$$\text{Given, } \vec{V} = V_m \angle \theta_v$$

$$\therefore V_m = 5 ; \theta_v = 30^\circ$$

$$Z = (4 - j2) \Omega = 4.472 \angle -26.57^\circ$$

$$\Rightarrow \frac{\vec{V}}{Z} = \frac{5 \angle 30^\circ}{4.472 \angle -26.57^\circ} = \vec{I}$$

$$\therefore \vec{I} = 1.118 \angle 56.57^\circ \text{ A}$$

$$I_m = 1.118 ; \theta_i = 56.57^\circ$$


$$\therefore P_{av} = \frac{1}{2} \times 5 \times 1.118 \cos(30 - 56.57^\circ)$$

$$P_{av} = 2.45 \text{ W} \Rightarrow \text{By source}$$


$\therefore$  W.R.T  $\angle$  will not absorbed by the Pwr

$$P_{av}(CR) = P_{av}(S \cos \theta) = 8.5 \text{ W}$$

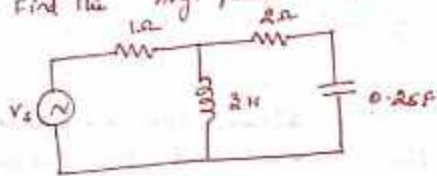(25) Assuming that  $V_s = 8 \cos(2t - 40^\circ) \text{ V}$  in the below circuit. Find the Avg. power delivered to  $2\Omega$  R.



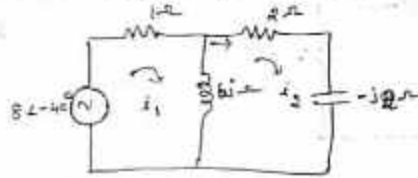Solution: Draw the circuit in frequency domain



To find P<sub>av</sub>, we need find  $i_2$  through  $2\Omega$  (2j)

$$\begin{bmatrix} 1+j0 & -kj \\ -kj & 2+j4 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 8\angle-40^\circ \\ 0 \end{bmatrix}$$

$$\Delta_2 = \begin{vmatrix} 1+j0 & 8\angle-40^\circ \\ -kj & 0 \end{vmatrix}$$

$$= kj(8\angle-40^\circ) = 6\angle 90^\circ (8\angle-40^\circ)$$

$$= 48\angle 50^\circ$$

$$\Delta = \begin{vmatrix} 1+j0 & -kj \\ -kj & 2+j4 \end{vmatrix}$$

$$= (1+j0)(2+j4) + 36$$

$$= 2+j4+j18 - 36 + 36$$

$$= 2+j22$$

$$= 19.78\angle 45^\circ$$

$$\therefore i_2 = \frac{\Delta_2}{\Delta} = \frac{48\angle 50^\circ}{19.78\angle 45^\circ}$$

$$i_2 = 2.43\angle 5^\circ \Rightarrow \text{through } 2\Omega$$

$$\therefore P_{av} = \frac{1}{2} \times I_m^2 \times R$$

$$= (2.43\angle 5^\circ)^2 = (2.43\angle 5^\circ)(2.43\angle 5^\circ)$$

$$P_{av} = 5.48\angle 10^\circ \text{ W}$$

$$P_{av} = (5.06\angle 10^\circ) \text{ W}$$

Apparent Power and Power factor

$$\text{Average power} \Rightarrow P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$P_{av} = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

$$\text{Apparent power} = V_{rms} I_{rms}$$

$$\therefore P_{av} = S \cos(\theta_v - \theta_i) \rightarrow \text{power factor}$$

$$= S \times \text{power factor}$$

$$(or) \Rightarrow \text{power factor} = \frac{P_{av}}{S}$$

$$\cos(\theta_v - \theta_i) = \frac{P_{av}}{S}$$

PF angle

$$\text{If purely 'R', } \therefore \theta_v = \theta_i \Rightarrow \cos 0^\circ = \frac{P_{av}}{S}$$


$$\Rightarrow S = P_{av}$$

If purely reactive load:  $\theta_v - \theta_i = \pm 90^\circ$

$$\therefore \cos(\pm 90^\circ) = \frac{P_{av}}{S}$$

$$\Rightarrow 0 = \frac{P_{av}}{S} \Rightarrow \boxed{P_{av} = 0}$$

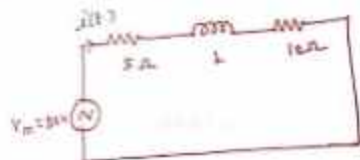26) In the circuit shown in the given figure, if the P consumed by the 5Ω R is 10W, what is the power factor of the circuit.



Solution:

$$PF = \frac{P_{av}}{S} = \frac{P_R + P_L + P_C}{V_{rms} I_{rms}} = \frac{10 + 0 + P_{10}}{50/\sqrt{2} \times I_{rms}}$$

Given,  $P_R = 10$

$$I_{rms}^2 \times 5 = 10 \quad [\because I_{rms}^2 R = 10]$$

$$I_{rms} = 2 \Rightarrow I_{rms} = \sqrt{2} = 1.414A = \underline{\underline{\sqrt{2}A}}$$

$$P_{10} = (\sqrt{2})^2 \times 10$$

$$= 20W$$

$$\therefore PF = \frac{10 + 20}{50 \times \sqrt{2}} = \frac{30}{50} = \underline{\underline{0.6}}$$

$$\boxed{PF = 0.6}$$

Definition of Apparent power (S):

$$\boxed{S = V_{rms} I_{rms}}$$

